

Dale Wheat
14 September 2019
Dallas Makerspace

Charlieplexing LEDs with Arduino

Introduction

- This class will introduce you to some methods of controlling LEDs using an Arduino
- We'll start with simple LED blinking projects and work our way up to more complex arrangements
- No previous Arduino experience is required
- No previous electronics experience is required

Course Outline

- Introduction
- Software setup
- Exercise 1: Blink a single LED
- Exercise 2: Blink an external LED
- Exercise 3: Active low LEDs
- Exercise 4: Blink using a different pin
- Review
- Exercise 6: Multiplexing techniques
- Exercise 7: Cheating
- Exercise 8: Charlieplexing LEDs

Software Setup

- Install Arduino IDE software on participant's laptops
- Install device driver software (if necessary)
 - CH341SER.EXE
- Install LEDstick library
- Distribute Arduino UNOs + USB cables

Set up your Arduino

- Plug the Arduino Uno into your laptop using the USB cable provided
- Open the Arduino IDE software
- Select menu item “Tools -> Board -> Arduino/Genuino Uno”
- Select menu item “Tools -> Port -> COM4”
 - Your COM port number may be (probably is) different
 - Just pick the last (or highest numbered) port available

Install the LEDstick library


- TODO <instructions>

Exercise 1: Verify “Blink” sketch works

- Select menu item “File -> Examples -> 01.Basics -> Blink”
- Select menu item “Sketch -> Verify/Compile”
 - Look for “Done compiling.” status message
- Select menu item “Sketch -> Upload”
 - Look for “Done uploading.” status message
- Does it blink?

Schematic Diagram

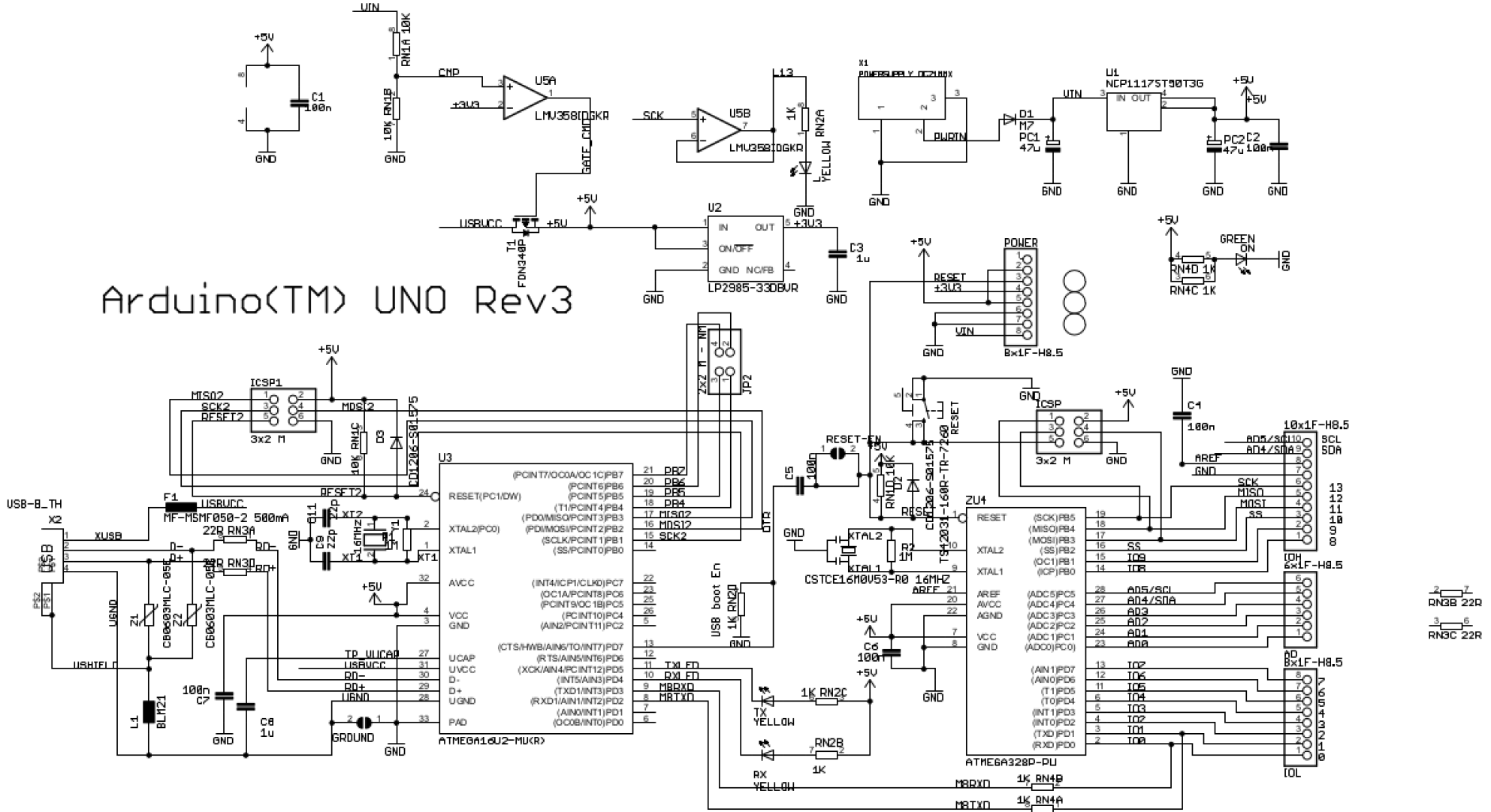• https://www.arduino.cc/en/uploads/Main/Arduino_Uno_Rev3-schematic.pdf




Arduino(TM) UNO Rev3



Schematic Diagram

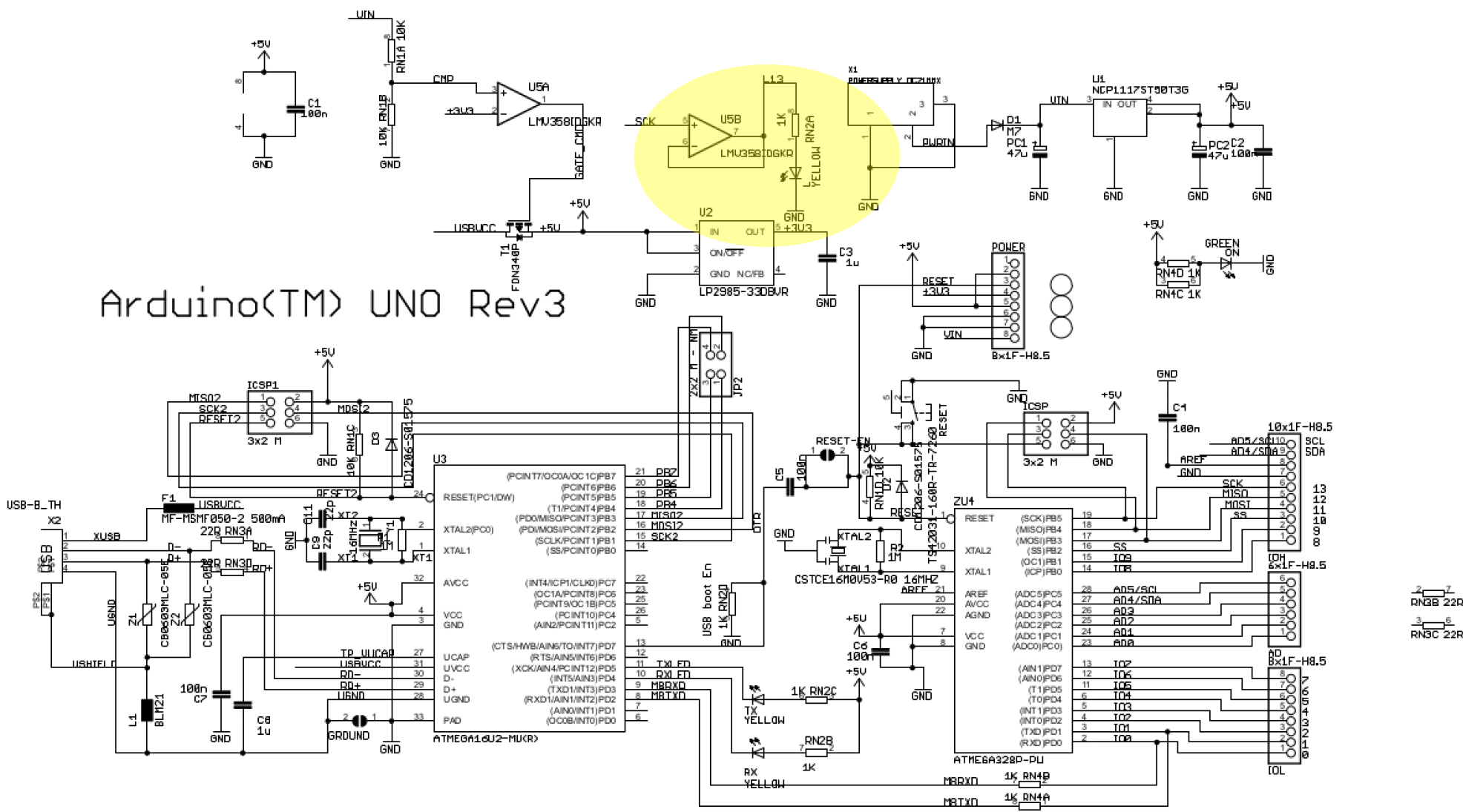
• https://www.arduino.cc/en/uploads/Main/Arduino_Uno_Rev3-schematic.pdf



Arduino(TM) UNO Rev3



Schematic, partial

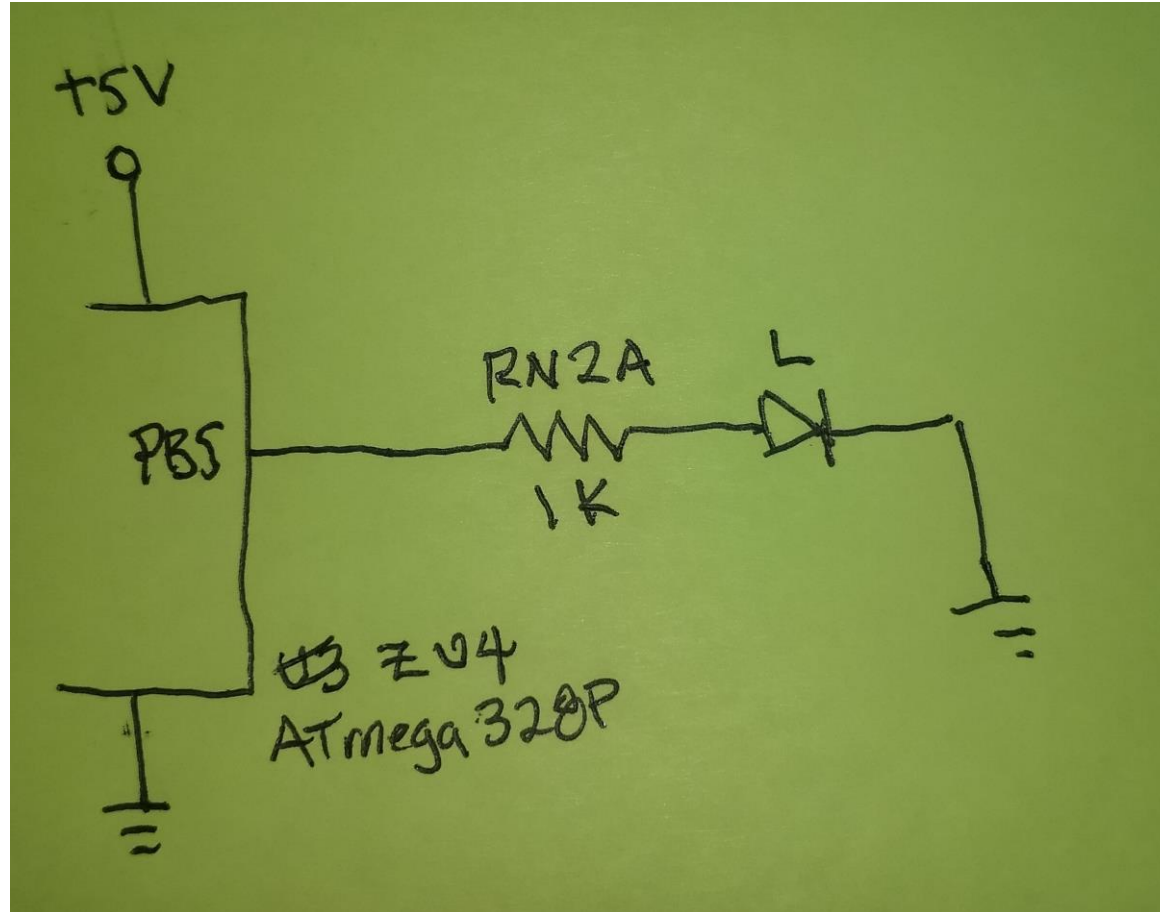

Analysis of “Blink” sketch

```
void setup() {  
    pinMode(LED_BUILTIN, OUTPUT);  
}
```

```
void loop() {  
    digitalWrite(LED_BUILTIN, HIGH); // LED on  
    delay(1000); // short delay  
    digitalWrite(LED_BUILTIN, LOW); // LED off  
    delay(1000); // short delay  
}
```

Analysis of “Blink” sketch

```
void setup() {  
    pinMode(LED_BUILTIN, OUTPUT);  
}
```

```
void loop() {  
    digitalWrite(LED_BUILTIN, HIGH); // LED on  
    delay(1000); // short delay  
    digitalWrite(LED_BUILTIN, LOW); // LED off  
    delay(1000); // short delay  
}
```

Analysis of “Blink” sketch

```
void setup() {  
  pinMode(LED_BUILTIN, OUTPUT);  
}
```

```
void loop() {  
  digitalWrite(LED_BUILTIN, HIGH); // LED on  
  delay(1000); // short delay  
  digitalWrite(LED_BUILTIN, LOW); // LED off  
  delay(1000); // short delay  
}
```

Analysis of “Blink” sketch

```
void setup() {  
  pinMode(LED_BUILTIN, OUTPUT);  
}
```

```
void loop() {  
  digitalWrite(LED_BUILTIN, HIGH); // LED on  
  delay(1000); // short delay  
  digitalWrite(LED_BUILTIN, LOW); // LED off  
  delay(1000); // short delay  
}
```

Analysis of “Blink” sketch


```
void setup() {  
  pinMode(LED_BUILTIN, OUTPUT);  
}
```

```
void loop() {  
  digitalWrite(LED_BUILTIN, HIGH); // LED on  
  delay(1000); // short delay  
  digitalWrite(LED_BUILTIN, LOW); // LED off  
  delay(1000); // short delay  
}
```

Exercise 2: Blink an external LED

- Use the same “Blink” sketch
- Disconnect the Arduino Uno from the laptop
- Connect external LED between D13 and GND
 - Connect red wire (anode) to D13
 - Connect black wire (cathode) to GND
- Reconnect the Arduino Uno to the laptop
- Observe that the external LED blinks in sync with the on-board LED
- These LEDs are connected in parallel


Schematic

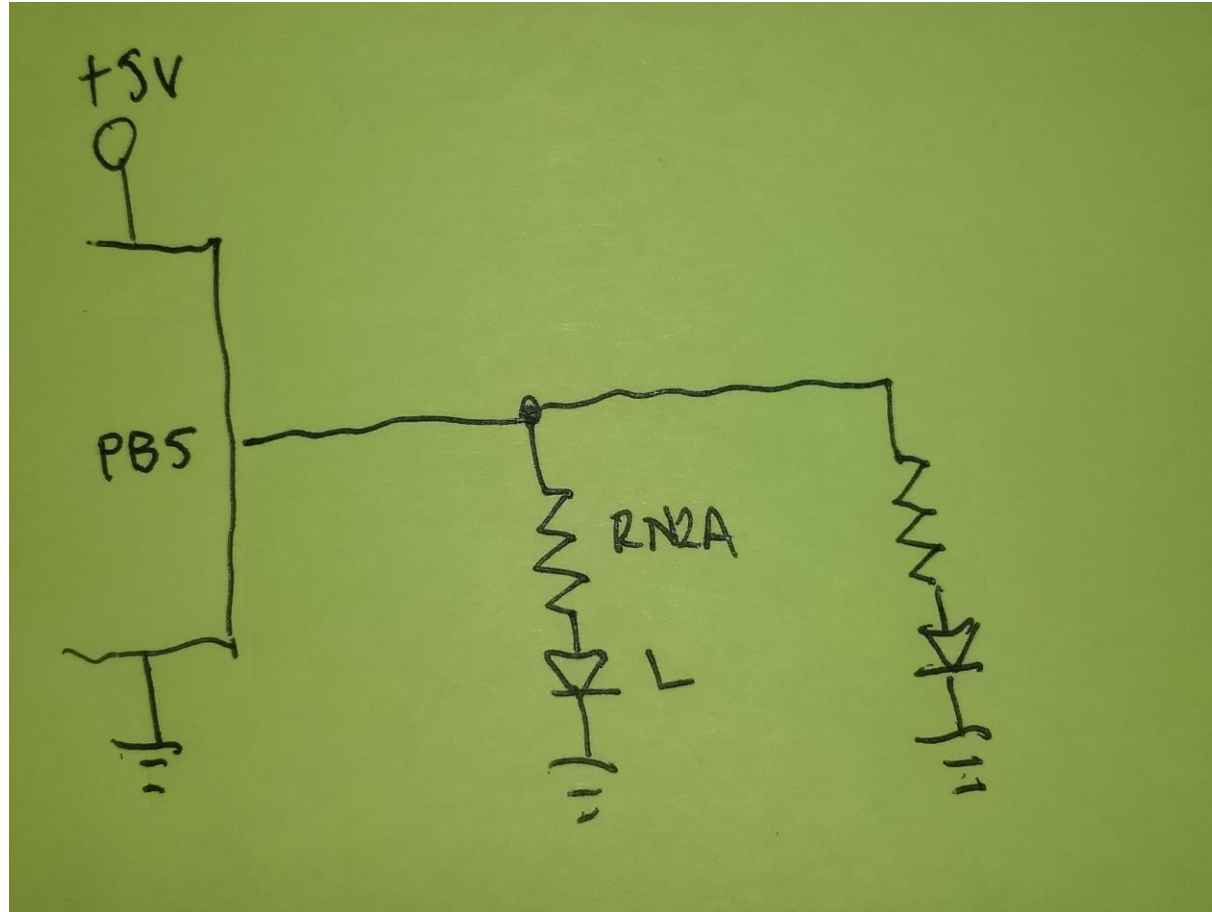

Exercise 3: Active low LEDs

- The LED on the Arduino board is connected as “active high”
- This means that the LED is active (on) when the driving signal is high
- Another method is “active low”
- The LED is “reversed” in the circuit and active when the signal is low
- Disconnect the Arduino Uno from the laptop
- Connections:
 - Connect the red wire to 5V
 - Connect the black wire to D13
- Reconnect the Arduino Uno to the laptop
- Observe a different blinking pattern

Schematic

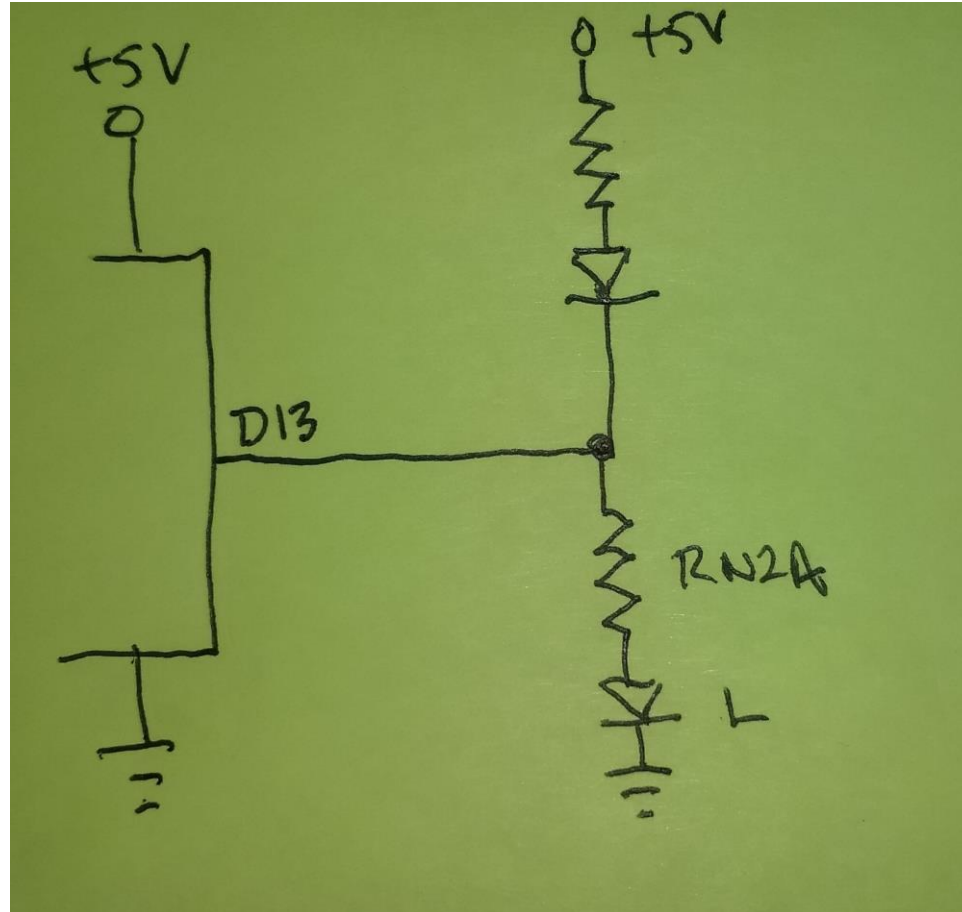

Connections

- Disconnect the Arduino Uno from the laptop
- Connect the 2nd external LED (if available) between D2 and GND
 - Connect the red wire to D2
 - Connect the black wire to GND
- Reconnect the Arduino Uno to the laptop
- Compile and upload the modified sketch
 - Select the menu item “Sketch -> Verify/Compile”
 - Select the menu item “Sketch -> Upload”
- Verify correct blinking pattern

Exercise 4: Blink using a different pin

- Open and run the “blink_2” example sketch:
 - Select menu item “File -> Examples -> LEDstick -> blink_2”
 - Select menu item “Sketch -> Verify/Compile”
 - Look for “Done compiling.” status message
 - Select menu item “Sketch -> Upload”
 - Look for “Done uploading.” status message
 - Does it blink?

Review

- Blinking single LEDs with Arduino turns out to be simple
- The method we used in the previous exercise is called “direct drive”
- One output pin is used to drive one or more LEDs
- How many LEDs can you blink independently with an Arduino Uno?
 - Using digital pins D2-D13: 12 LEDs
 - Using analog pins A0-A5: 6 LEDs
 - Total: 18 LEDs
- The Arduino Mega 2560 has more I/O pins and can blink more LEDs
 - The device is limited to a maximum of 200 mA total, or about 10 LEDs



Exercise 6: Multiplexing techniques

- I/O expanders & shift registers
- Digit/segment LED displays
- Row/column LED displays




I/O Expanders & Shift Registers

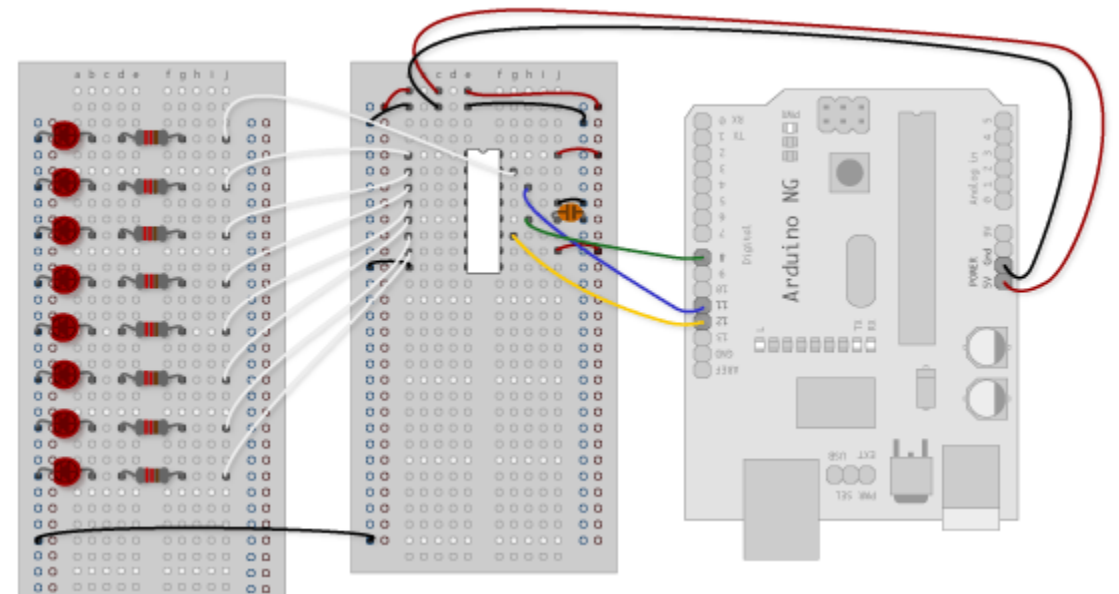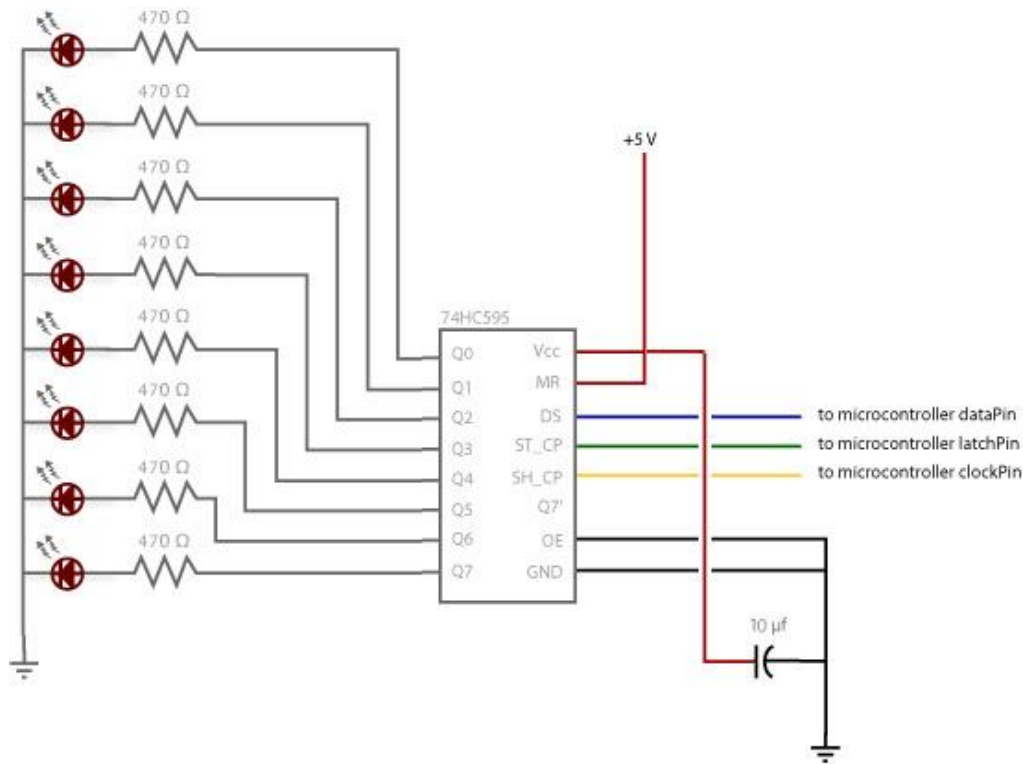- Using just a small number of control lines, more outputs can be used
- From <https://www.arduino.cc/en/Tutorial/ShiftOut>



Single Digit/Segment Displays

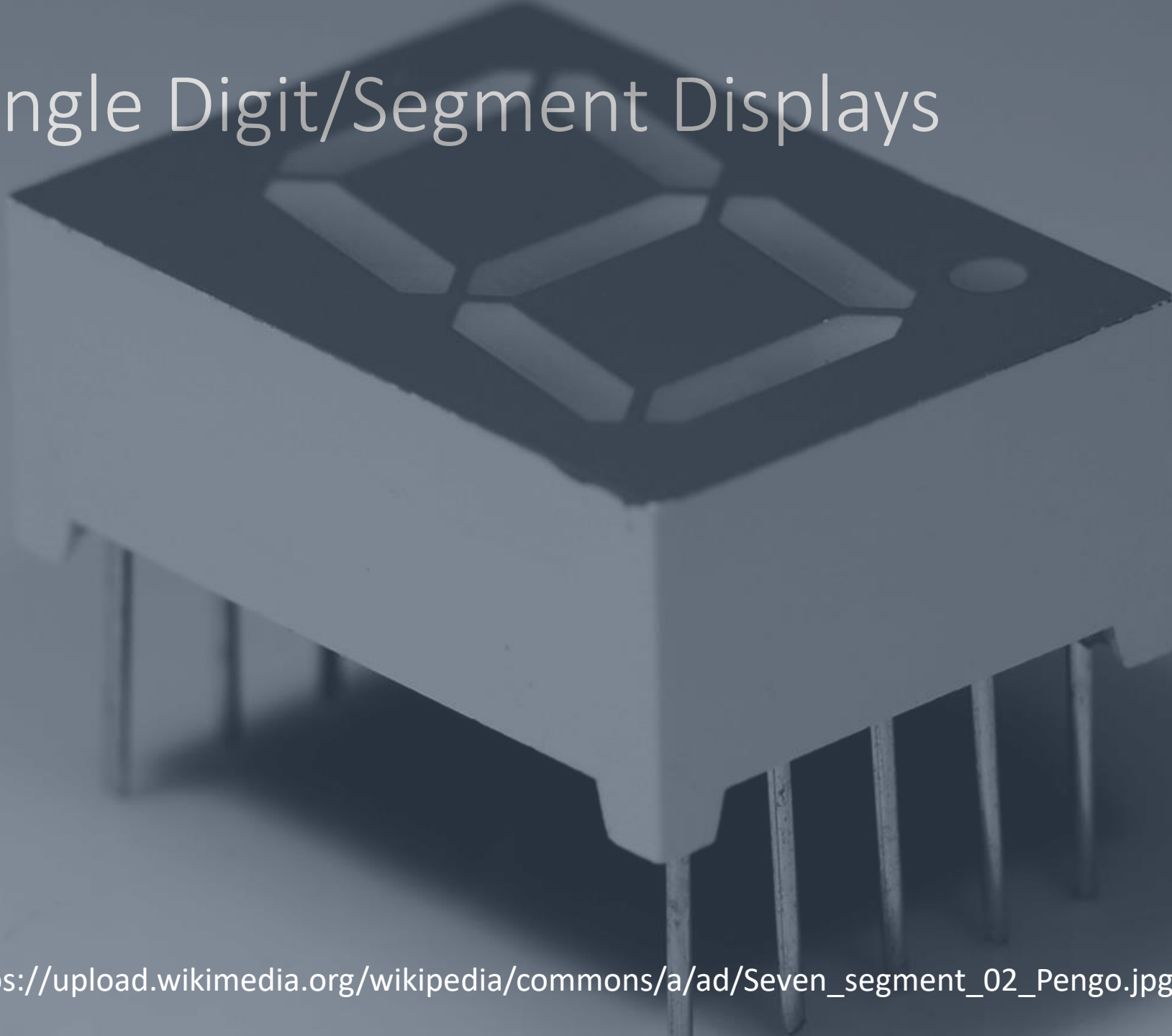


► https://upload.wikimedia.org/wikipedia/commons/a/ad/Seven_segment_02_Pengo.jpg

Multi-Digit/Segment LED Displays


<https://www.adafruit.com/product/1264>




KW4-12041ALA

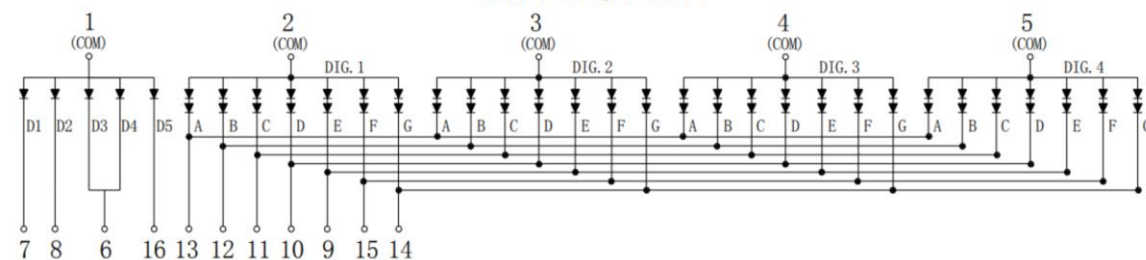


KW4-12041CLA

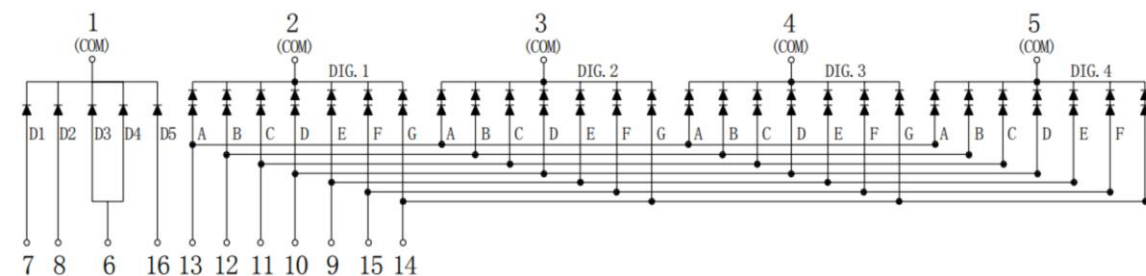


Row/Column LED Displays

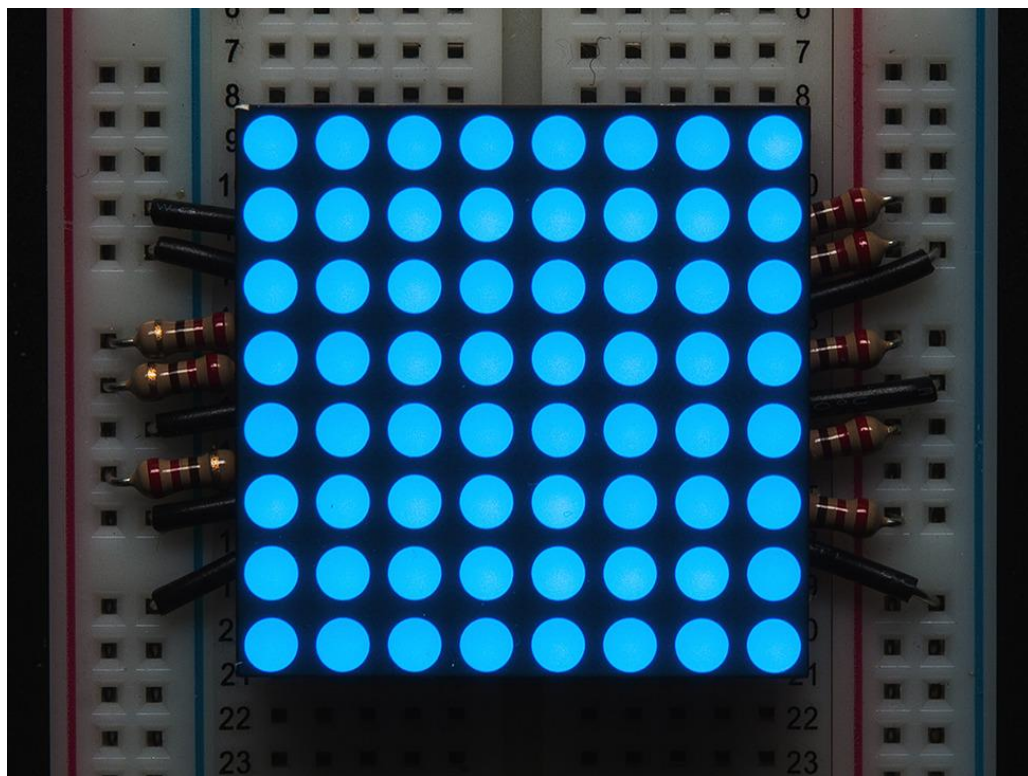

KWM-R30881ABB

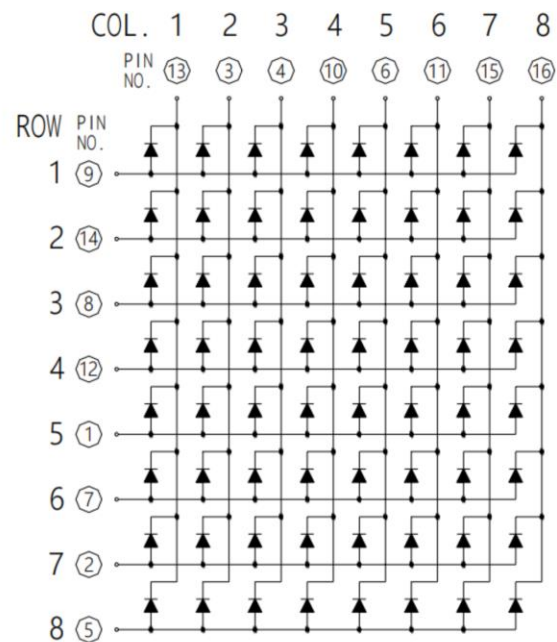

KWM-R30881CBB

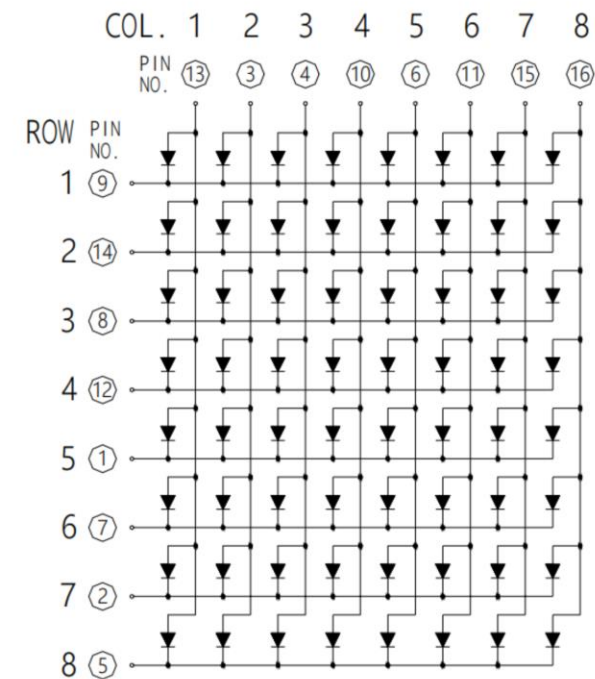

Exercise 7: Cheating

- Larson scanner
 - Connect tinyCylon to 5V and GND – no sketch required
- NeoPixels
 - Connect 5V, GND & D6 – run “strandtest” sketch
- MAX7219 multiplexer chip with 8x8 LED array
 - Connect 5V, GND, D4 -> DIN, D5 -> CS, D6 -> CLK – run “_8x8_node” sketch

Exercise 8: Charlieplexing LEDs


- Background
- Schematics
- Exercises with the 12LEDstick
- Advantages & disadvantages
- Examples
 - Smart Battery Meter
 - 12LEDcircle
 - Geophone 12
 - 12LEDstick
 - LolShield

Background

- “Charlieplexing is a technique for driving a multiplexed display in which relatively few I/O pins on a microcontroller are used e.g. to drive an array of LEDs.”
- “Charlieplexing was proposed in early 1995 by Charlie Allen at Maxim Integrated”
--<https://en.wikipedia.org/wiki/Charlieplexing>
- Charlieplexing can address $n \times (n-1)$ LEDs, where n = number of pins.
- Each pin must be able to output high & low levels
- Each pin must also be able to be tri-stated, or turned into an input.


Schematics

Simplest configuration (two nodes)

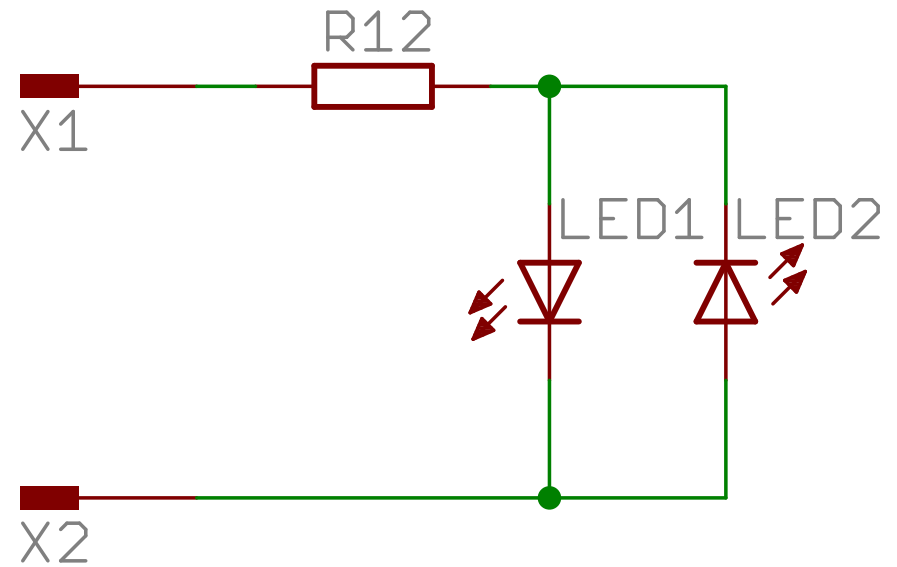


Schematics, continued


Three pin configuration

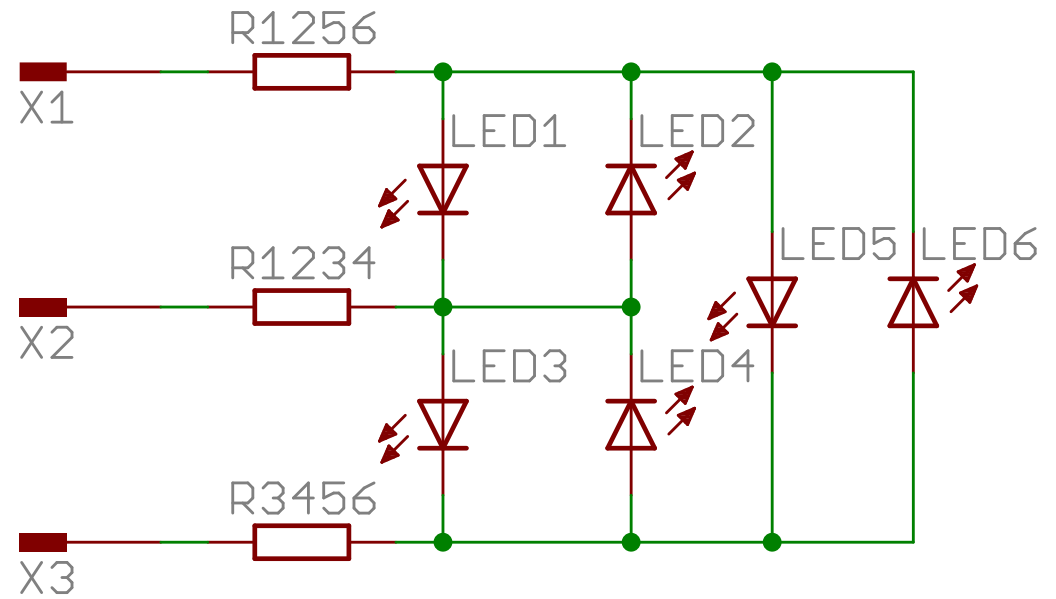

Schematics,
correct but
not helpful

Four wire configuration
(12LEDstick)

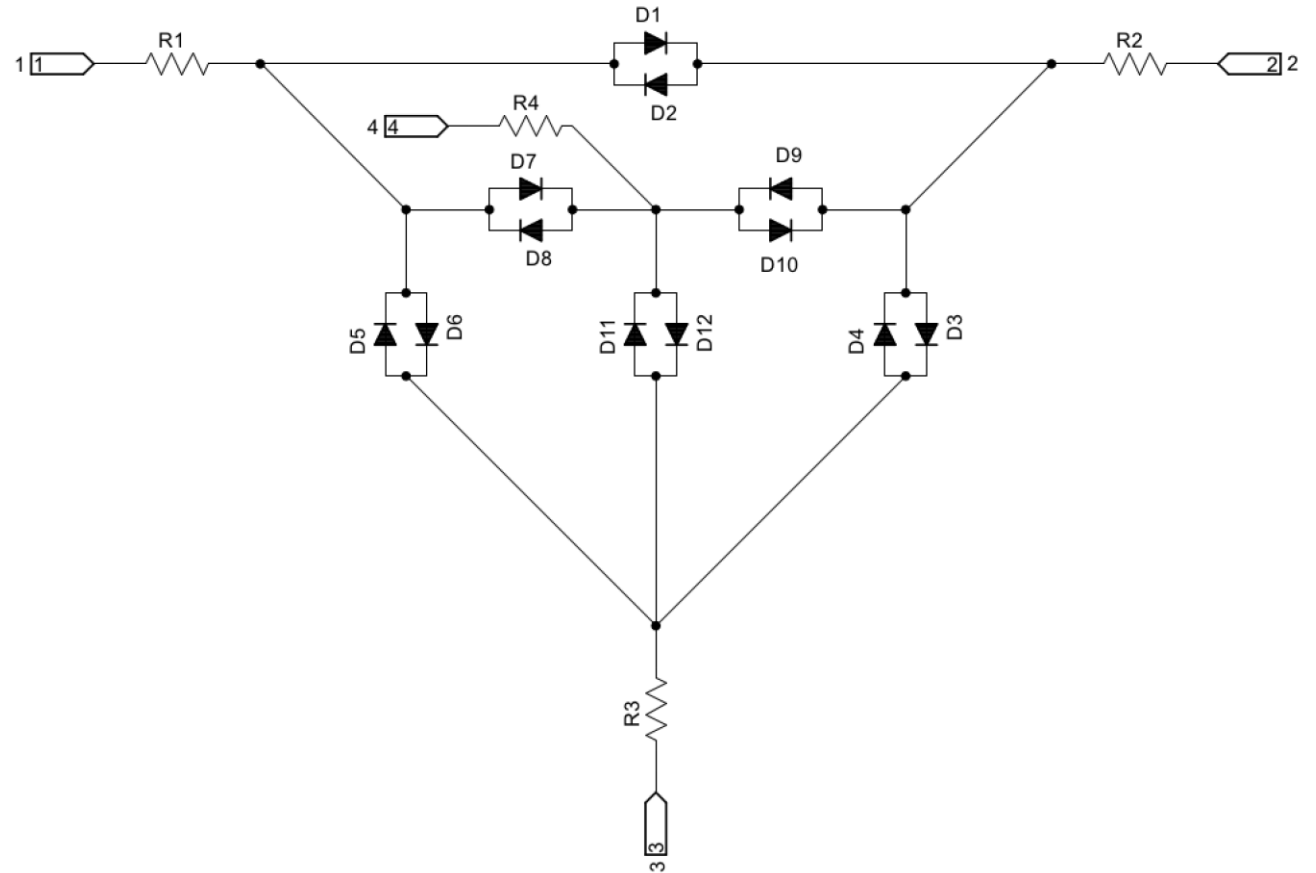

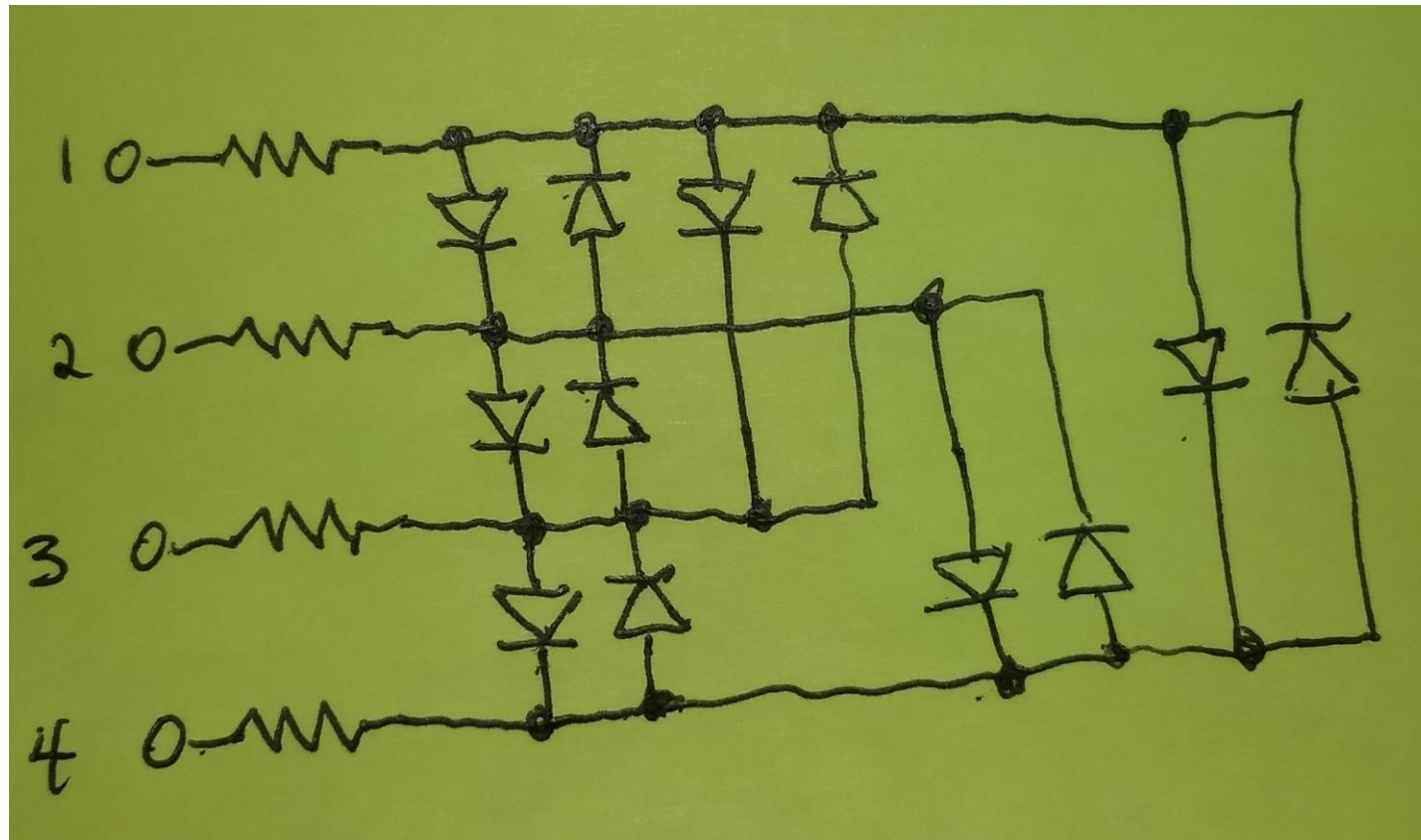


Schematic, hopefully a bit clearer

Four wire configuration

Schematic, six pin configuration

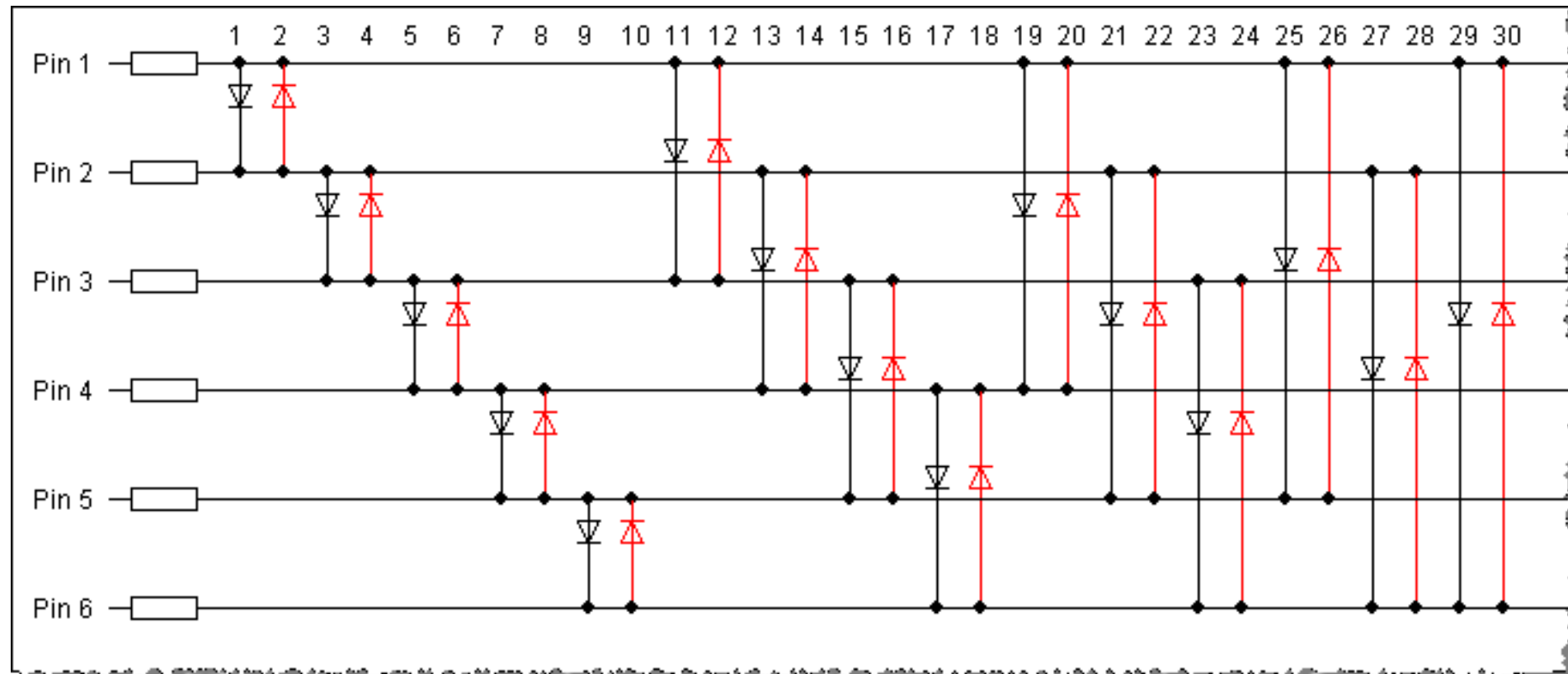
- From <https://forum.arduino.cc/index.php?topic=53329.0>



Install the 12LEDstick


- Unplug the Arduino Uno from the laptop
- Install the 12LEDstick in pins D2, D3, D4 & D5
- Reconnect the Arduino Uno to the laptop

Charlieplexing the hard way: 2 LEDs

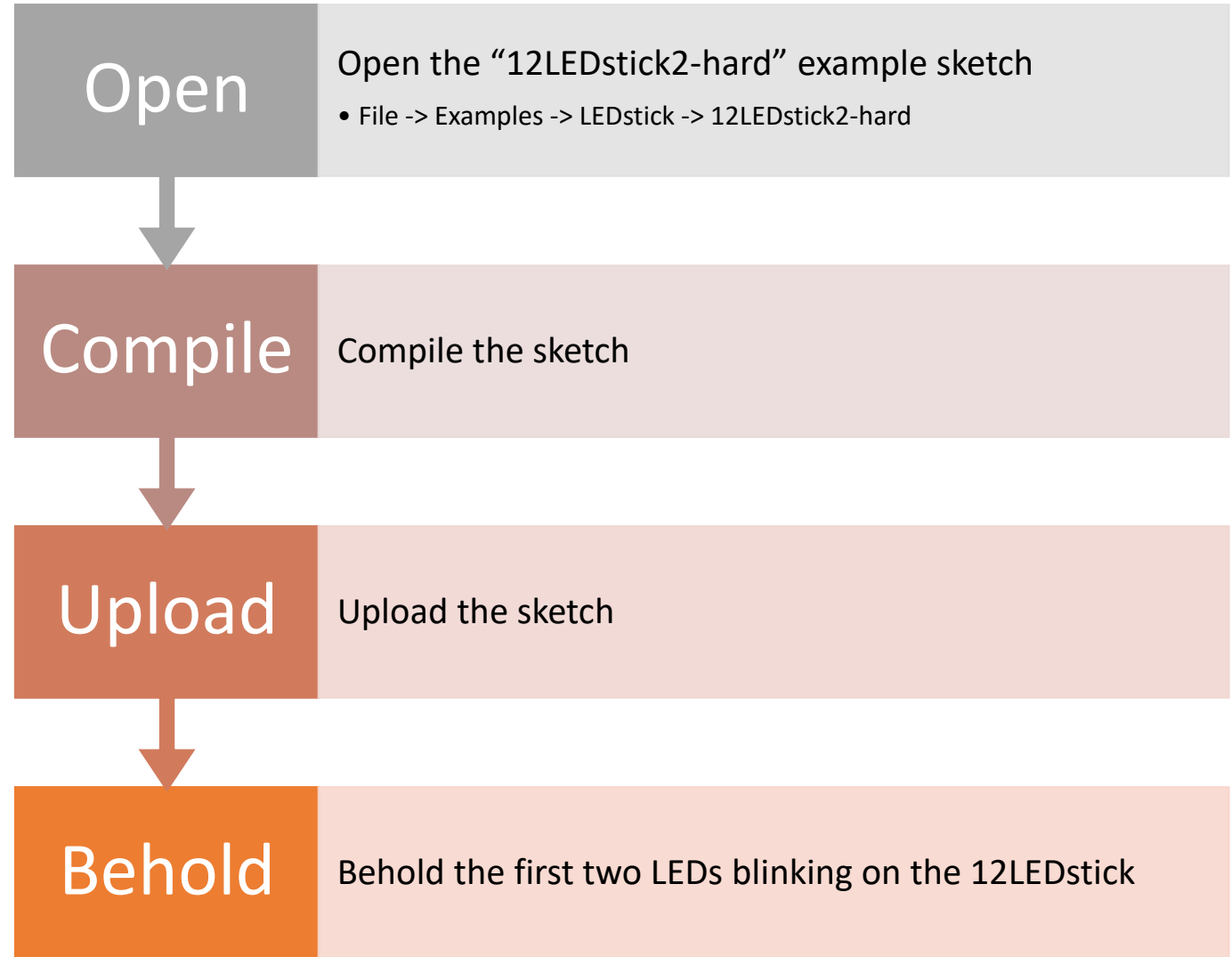


12LEDstick2-hard Sketch
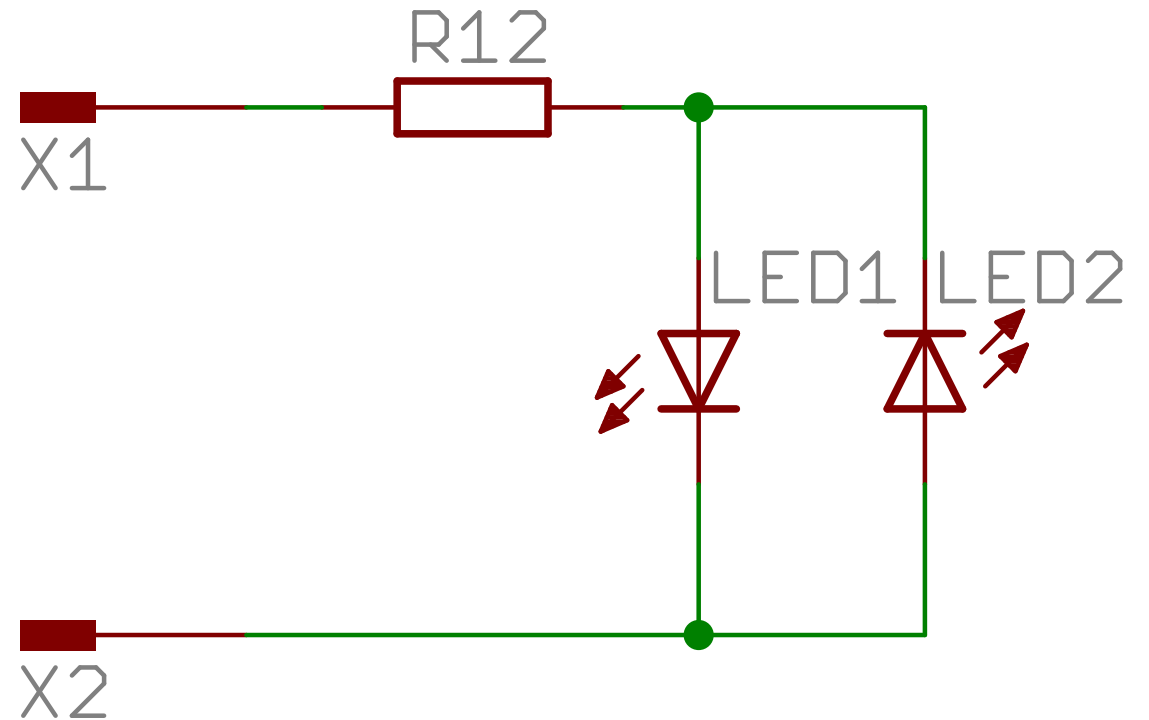
```
void setup() {  
  pinMode(2, OUTPUT);  
  pinMode(3, OUTPUT);  
}  
  
void loop() {  
  digitalWrite(2, HIGH);  
  digitalWrite(3, LOW);  
  delay(250); // short delay  
  digitalWrite(2, LOW);  
  digitalWrite(3, HIGH);  
  delay(250); // short delay  
}
```



Charlieplexing the hard way: 6 LEDs

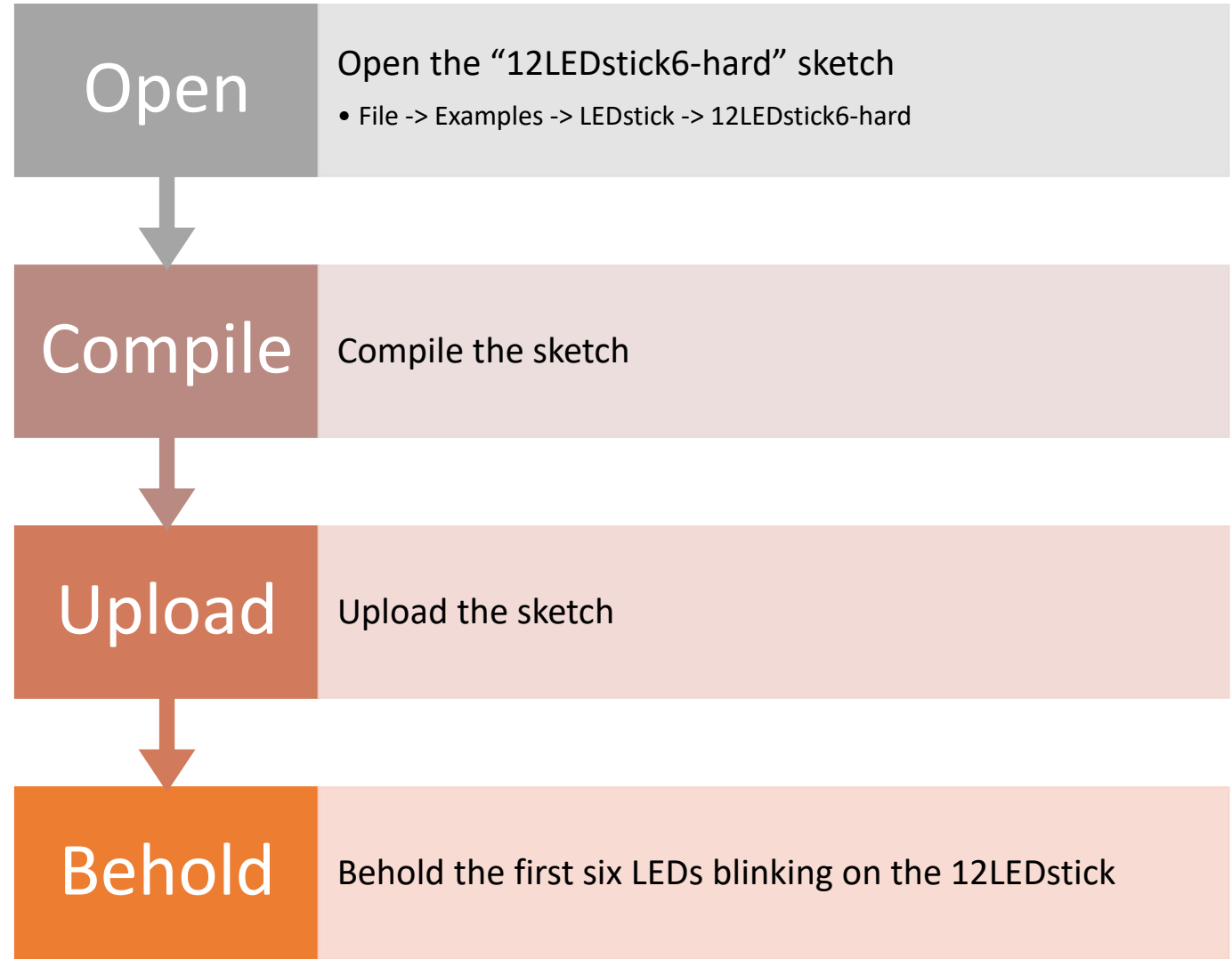

12LEDstick6-hard Sketch

```
void setup() {
  // none needed
}

void loop() {
  // LED 1 on (1->2)
  pinMode(2, OUTPUT);
  pinMode(3, OUTPUT);
  pinMode(4, INPUT);
  digitalWrite(2, HIGH);
  digitalWrite(3, LOW);
  digitalWrite(4, LOW);
  delay(250);

  // LED 2 on (2->1)
  pinMode(2, OUTPUT);
  pinMode(3, OUTPUT);
  pinMode(4, INPUT);
  digitalWrite(2, LOW);
  digitalWrite(3, HIGH);
  digitalWrite(4, LOW);
  delay(250);

  // LED 3 on (2->3)
  pinMode(2, INPUT);
  pinMode(3, OUTPUT);
  pinMode(4, INPUT);
  digitalWrite(2, HIGH);
  digitalWrite(3, LOW);
  digitalWrite(4, LOW);
  delay(250);

  // LED 4 on (3->2)
  pinMode(2, INPUT);
  pinMode(3, OUTPUT);
  pinMode(4, OUTPUT);
  digitalWrite(2, LOW);
  digitalWrite(3, LOW);
  digitalWrite(4, HIGH);
  delay(250);

  // LED 5 on (3->1)
  pinMode(2, OUTPUT);
  pinMode(3, INPUT);
  pinMode(4, OUTPUT);
  digitalWrite(2, LOW);
  digitalWrite(3, LOW);
  digitalWrite(4, HIGH);
  delay(250);

  // LED 6 on (1->3)
  pinMode(2, OUTPUT);
  pinMode(3, INPUT);
  pinMode(4, INPUT);
  digitalWrite(2, HIGH);
  digitalWrite(3, LOW);
  digitalWrite(4, LOW);
  delay(250);

  // all LEDs off
  pinMode(2, INPUT);
  pinMode(3, INPUT);
  pinMode(4, INPUT);
  delay(250);
}
```


Using the LEDstick Arduino Library

- Load the “12LEDstick.ino” sketch
 - File -> Examples -> LEDstick -> 12LEDstick
- Compile+Upload the sketch to the Arduino Uno (the usual way)
- Behold all twelve LEDs blinking in sequence

12LEDstick Sketch

```
#include <LEDstick.h>
LEDstick stick(2, 3, 4, 5); // single instance, defining pins used

void setup() {
  // no special setup needed when using the LEDstick library
}


void loop() {
  // Light up each of the 12 LEDs one at a time
  // Asking for LED 0 means to turn them all off
  for(int i = 0; i < 13; i++) {
    stick.led(i);
    delay(250); // short delay
  }
}
```

Advantages & Disadvantages

- Advantages:
 - Uses fewer pins
 - Requires fewer current-limiting resistors
- Disadvantages:
 - Not all LEDs can be lit at the same time
 - Requires quick refresh rate to simulate all LEDs on
 - Sometimes hard to isolate defective LEDs
 - Hardware layout can be more complex
 - Software can become more complex


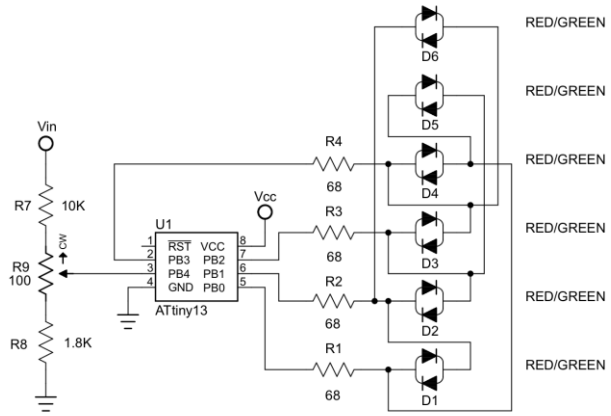
Examples of Charlieplexed LED Displays

- Products developed by Dale Wheat
 - Smart Battery Meter
 - 12LEDcircle
 - Geophone 12
 - 12LEDstick
- LolShield by Jimmie P. Rogers






Smart Battery Meter

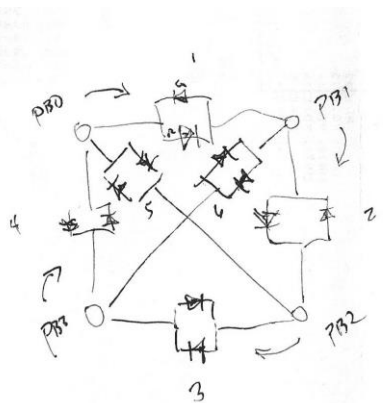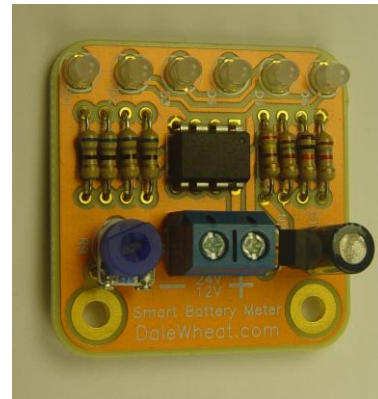- Featured in Circuit Cellar Magazine Issue 226 May 2009




12LEDcircle

 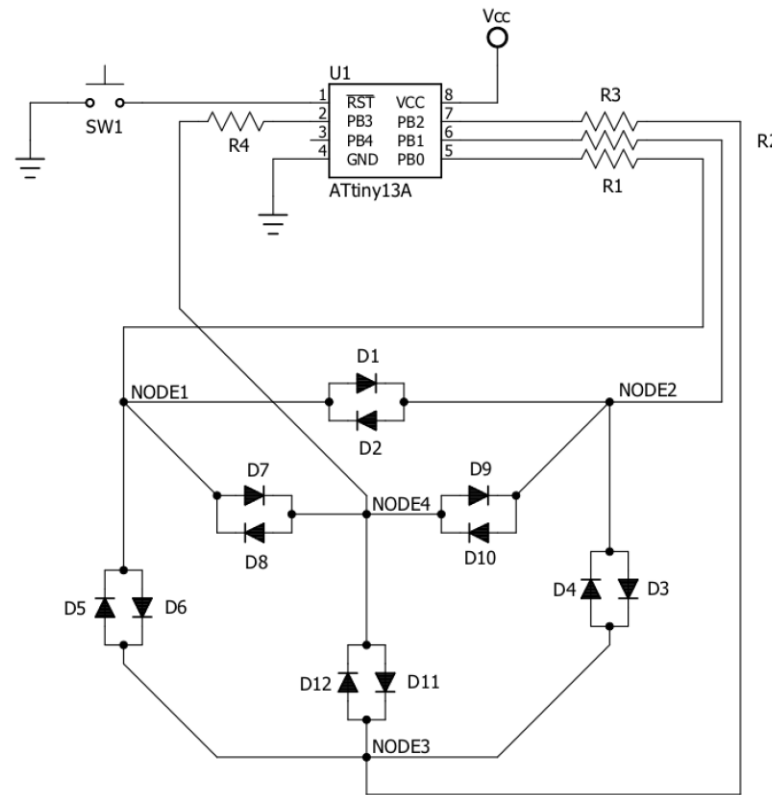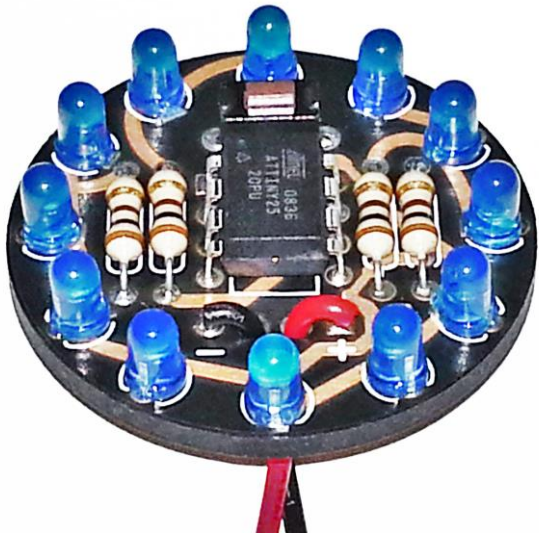

https://youtu.be/8I2yQX_0R4g


Geophone 12

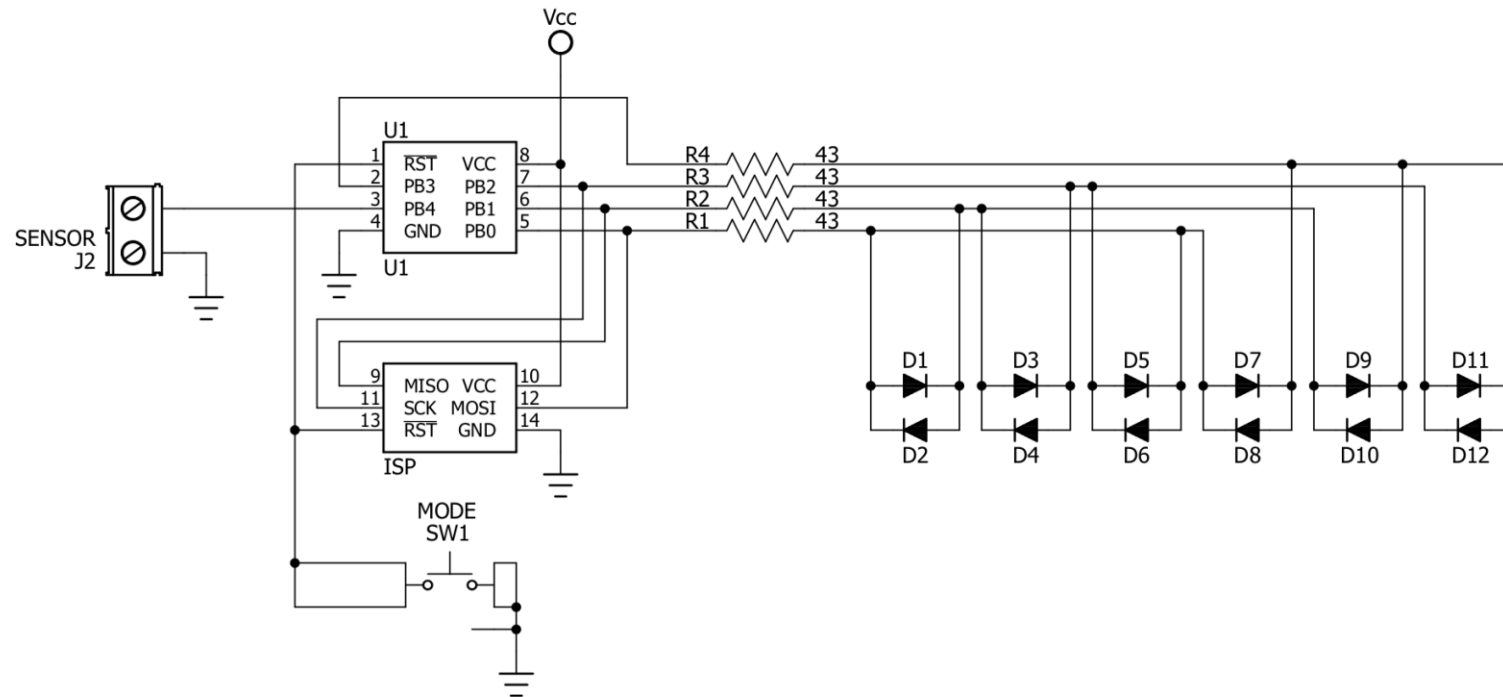

tia TECHNOLOGY IN ACTION™

Arduino Internals

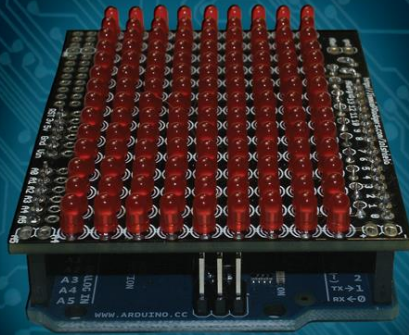LOOK INTO THE HEART OF YOUR
ARDUINO BOARD



Dale Wheat

LOLShield

- LOL = Lots of LEDs (126 to be exact)
- Designed by Jimmie P Rodgers
- Made the cover of my book

Conclusion

- There are lots of ways to blink LEDs with Arduinos
- Running out of pins does not mean running out of LEDs
- Charlieplexing requires a bit more thought up front



Thank you!

- I really appreciate you attending and participating in this class.
- Please let me know what other classes you would like to take.

Revision History

- Original version v1.0 – September 2019
- Revised to include library support – October 2019